

### **Instructions**

This assignment uses an online simulation to manipulate an electrical circuit. Afterward, you will write an explanation using Kirchhoff's laws (current rule and voltage rule aka junction rule and loop rule) for why your circuit successfully accomplishes the task.

Take a screenshot of the final result of each level (including an ammeter if necessary) and email all to Mrs. McKeon. Be sure to clearly label each screenshot with each level.

Go to the online PhET simulation called "Circuit Construction Kit: DC - Virtual Lab" found at <https://phet.colorado.edu/en/simulation/circuit-construction-kit-dc-virtual-lab>

### **Experiment**

Complete the following levels. Note that your circuit cannot be "on fire" for your circuit to count.

- 1) Make a light bulb light brightly using 4 batteries.
- 2) Add an on/off switch.
- 3) Make 3 light bulbs light brightly with all 3 with the same brightness (same power). In your screenshot, include the ammeter displaying the current through each bulb.
- 4) Have a switch that turns on/off 2 of the 3 bulbs.
- 5) Have a switch that turns on/off all 3 lights.
- 6) Make a circuit with one main on/off switch that will turn on/off all 3 bulbs, each with a different brightness. Use the non-contact Ammeter to display the current through each bulb.

### **Analysis**

Explain Kirchhoff's laws using your own words.

Using Kirchhoff's laws, write a paragraph explaining how circuit **3** works. Include any calculations (if any).

Using Kirchhoff's laws, write a paragraph explaining how circuit **6** works. Include any calculations (if any).